

Assignment 11

Solution to GATE EC2017, question 43

Perisetti Sai Ram Mohan Rao

IIIT Raichur

January 7, 2021

Table of Contents

1 Question

2 Solution

- Pretext
- Explanation
- State Transition Table
- Conclusion

3 Annexure

Question

The state diagram of Finite State Machine (FSM) designed to detect an overlapping sequence of three bits as shown in figure. The FSM has an input 'In' and an output 'Out'. The initial state of FSM is S_0 .

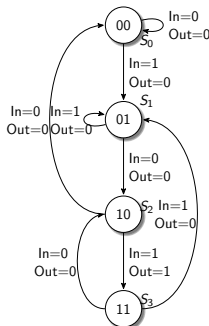


Figure:

If the input sequence is 10101101001101, starting with leftmost bit, then how many number of times 'Out' will be 1 is _____

Table of Contents


1 Question

2 Solution

- Pretext
- Explanation
- State Transition Table
- Conclusion


3 Annexure

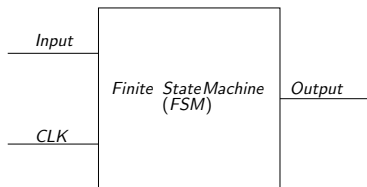We are required to find output sequence of Finite State Machine(FSM) and number 1's in output sequence.




If the CLK is not applied, there will be no difference between input sequence and the output sequence.

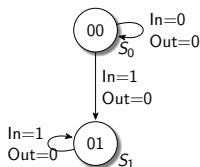The mechanism that should take place in Finite state machine is mentioned in Figure 1.



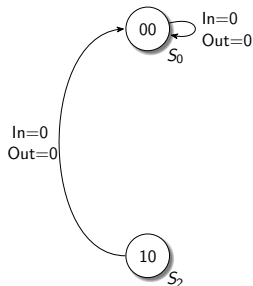In the finite machine we are required to find the output in current state for corresponding input. We have to see Input value at current state to get the Output. For example if we are at current state S_0 with input=1 then Output =0 and state changes to S_1 .



We are now looking at another example. If the current state of FSM is S_2 with input=0 then it gives output=0 and state changes to S_0 . We are required to find complete output sequence of FSM as stated in question. Which is made a table in next slide.

Solution / State Transition Table

State Transition Table			
Present state	Input	Next state	Output
S_0	1	S_1	0
S_1	0	S_2	0
S_2	1	S_3	1
S_3	0	S_2	0
S_2	1	S_3	1
S_3	1	S_1	0
S_1	0	S_2	0
S_2	1	S_3	1
S_3	0	S_2	0
S_2	0	S_0	0
S_0	1	S_1	0
S_1	1	S_1	0
S_1	0	S_2	1
S_2	1	S_3	1

Table: Table for States, Input and Output of finite state machine

Solution / Conclusion

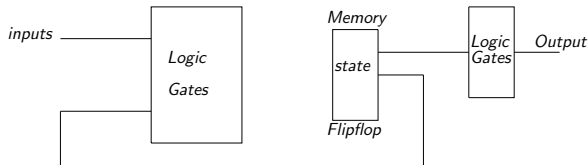


Figure:

Current State	S_0	S_1	S_2	S_3	S_2	S_3	S_1	S_2	S_3	S_2	S_0	S_1	S_1	S_2
Input	1	0	1	0	1	1	0	1	0	0	1	1	0	1
Output	0	0	1	0	1	0	0	1	0	0	0	0	0	1

Table: Table for States, Input and Output of finite state machine

The Output sequence of FSM is 00101001000001 from Table 1.

Then number of times 'Out' will be 1 is 4

Answer = 4

Table of Contents

1 Question

2 Solution

- Pretext
- Explanation
- State Transition Table
- Conclusion

3 Annexure

The behavior of state machines can be observed in many devices in modern society that perform a predetermined sequence of actions depending on a sequence of events with which they are presented.

- Vending machines, which dispense products when the proper combination of coins is deposited.
- Elevators, whose sequence of stops is determined by the floors requested by riders
- Traffic lights, which change sequence when cars are waiting.
- Combination locks, which require the input of a sequence of numbers in the proper order.

Thank you.